



Faculty of Engineering and Technology

Electrical and Computer Engineering Department

Digital Lab (ENCS2110)

Experiment No.1 Post-Lab

Title: Combinational Logic Circuits

Prepared by:

Name: Aya Dahbour

Number: 1201738


Instructor: Dr. Bilal Karaki

TA: Eng. Ali Hamoudeh

Post-lab questions' solution:

*All circuits were connected using Proteus.


1. $F=AB(CA)$ using AND gates

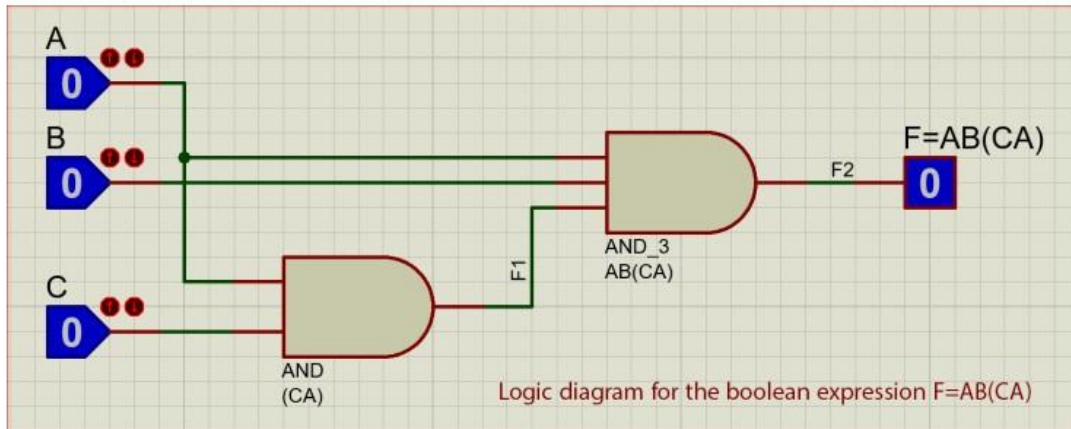

Figure(1): F logic diagram


- 2.

A. $F2 = (A+B)(CD+A)$

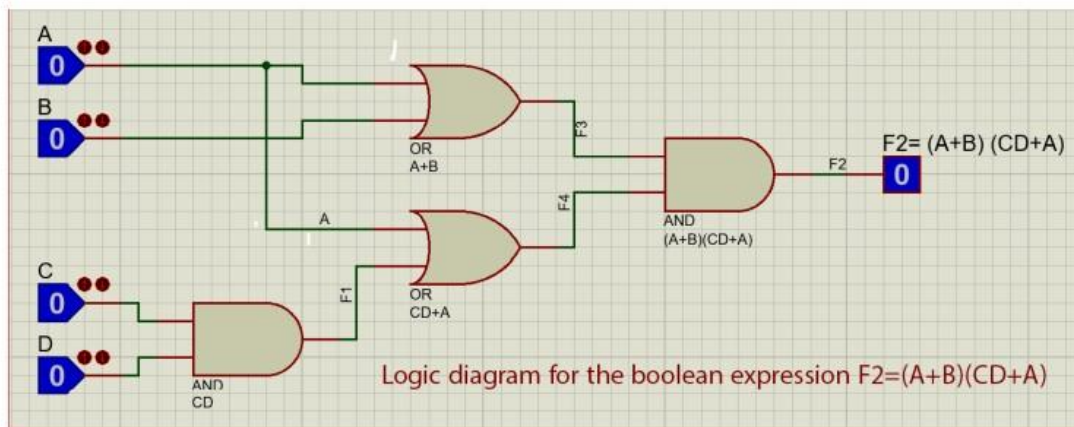

Figure(2): F2 logic diagram

B. $F3 = (ABC+D)C$

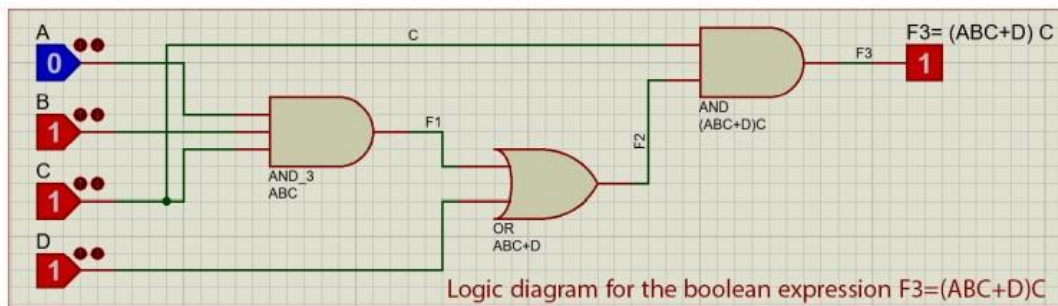


Figure(3): F3 logic diagram

3. OR operation implemented using AND, NOT gates.

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

Table(1): OR truth table

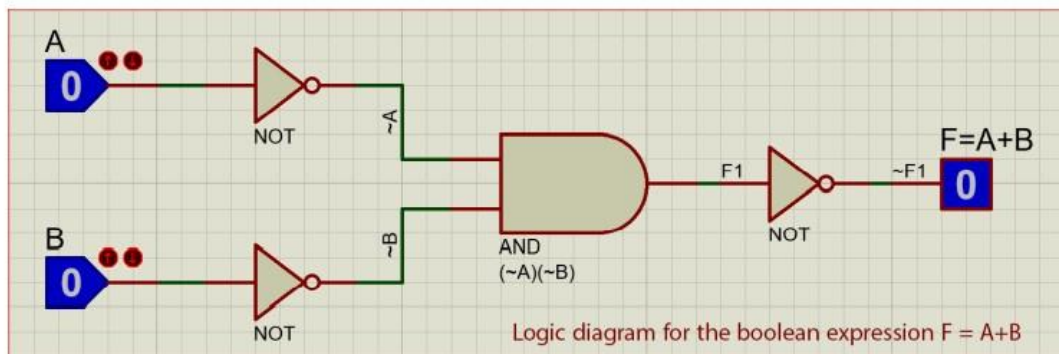


Figure(4): OR implementation using AND, NOT gates

4. AND gate implemented using OR, NOT gates.

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

Table(2): AND truth table

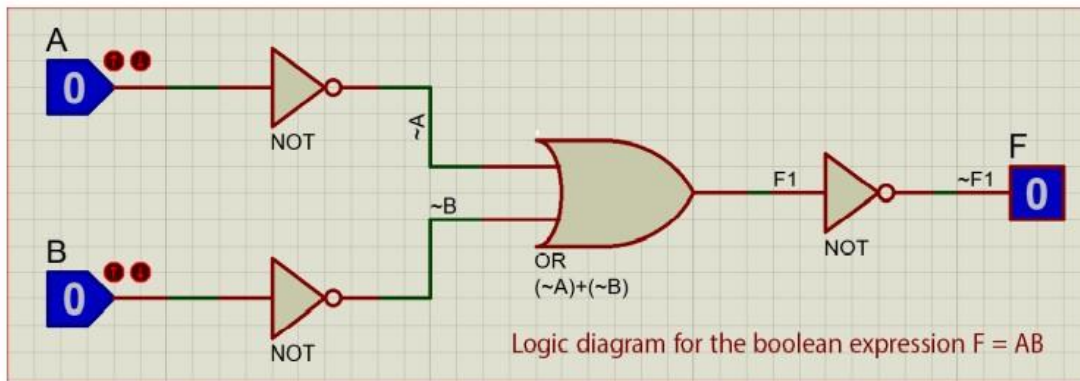

Figure(5): AND implementation using AND, NOT gates

5. Proving that XNOR is the inverse of XOR


$$\begin{aligned}
 F_1 &= AB + A'B' \Rightarrow \text{Xnor} \\
 F_2 &= AB' + A'B \Rightarrow \text{Xor (exclusive or)} \\
 F_1' &= (AB + A'B')' \\
 &= (AB)' \cdot (A'B')' \\
 &= (A' + B') \cdot (A + B) \Rightarrow \text{minterms (term 00, 11)} \\
 &\quad \left\{ \begin{array}{l} \text{equivalent to terms (01 and 10) in minterms} \\ \rightarrow = (AB') + (A'B) \end{array} \right. \quad \Downarrow \\
 &\quad F_1' = \Pi(0, 3) = \Sigma(1, 2) \\
 F_2 &= F_1'
 \end{aligned}$$

Figure(6): Proof of XNOR is inverse of XOR

6. NAND gate with four inputs implementation using two input NAND gates

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Table(3): 4-input NAND truth table

 

Figure(7): K-map for F


Using boolean algebra rules, I found equivalent boolean expression for the F which can be used to implement 4-input NAND using 2-input NANDs

$$\begin{aligned}
 F &= A' + B' + C' + D' \\
 &= (A' + B') + (C' + D')
 \end{aligned}$$

$$= (AB)' + (CD)'$$

$$= (((AB)')' \cdot ((CD)')')'$$

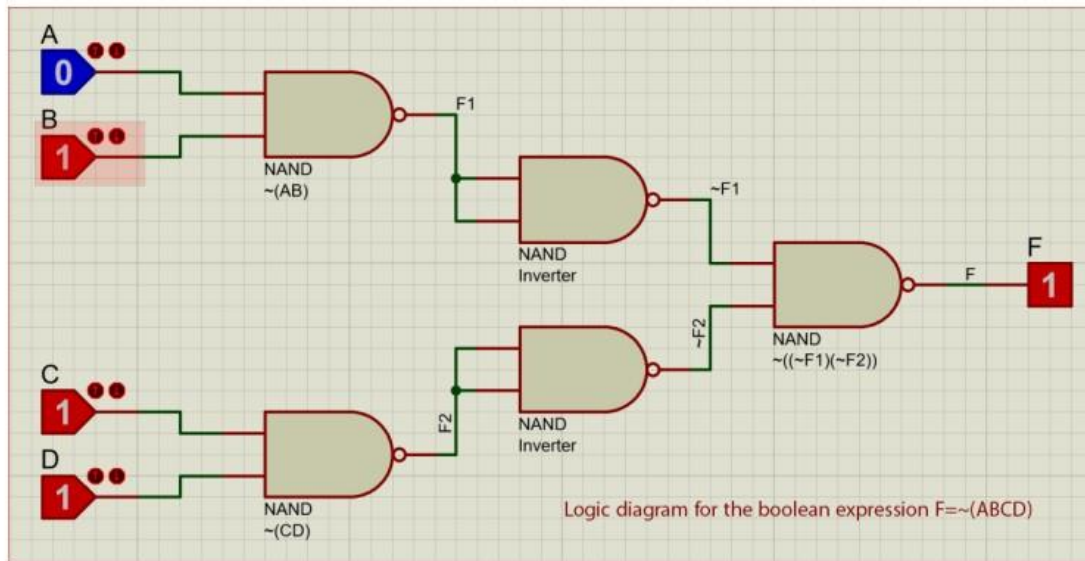This is the function which is going to be using in implementing 4-input NAND gate using 2-input NAND gates only.



Figure(8): 4-input NAND implementation using 2-input NAND


7.

$$A. F1 = A'BCD + ABCD' + A'BCD' + ABCD'$$

A	B	C	D	F1
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0


Table(4): F1 truth table

Using K-map:

 

Figure(9): K-map for F1

$$F1 = A'BC + BCD'$$

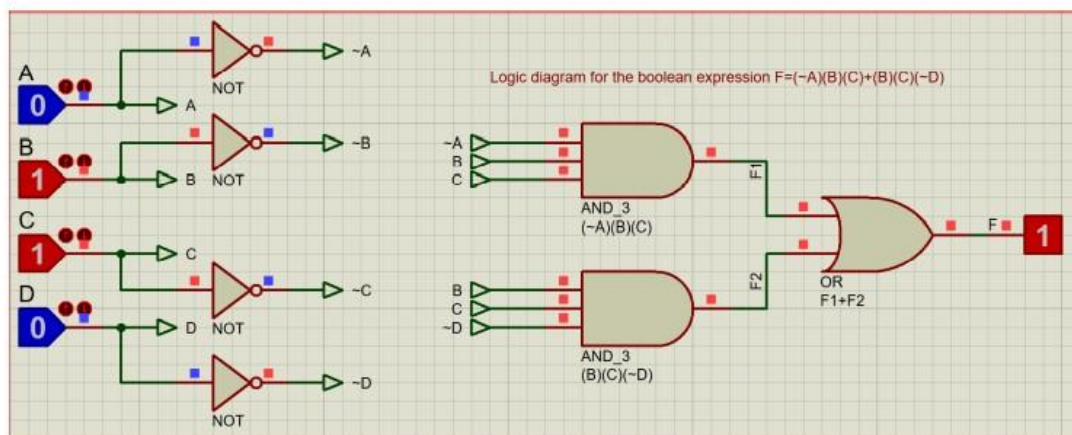


Figure(10): F1 logic diagram

$$B. F2 = A'B'C'D' + AB'CD' + A'B'CD' + A'BC'D'$$

A	B	C	D	F2
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0


Table(5): F2 truth table

Using K-map

 

Figure(11): K-map for F2

$$F2 = A'C'D' + B'CD'$$

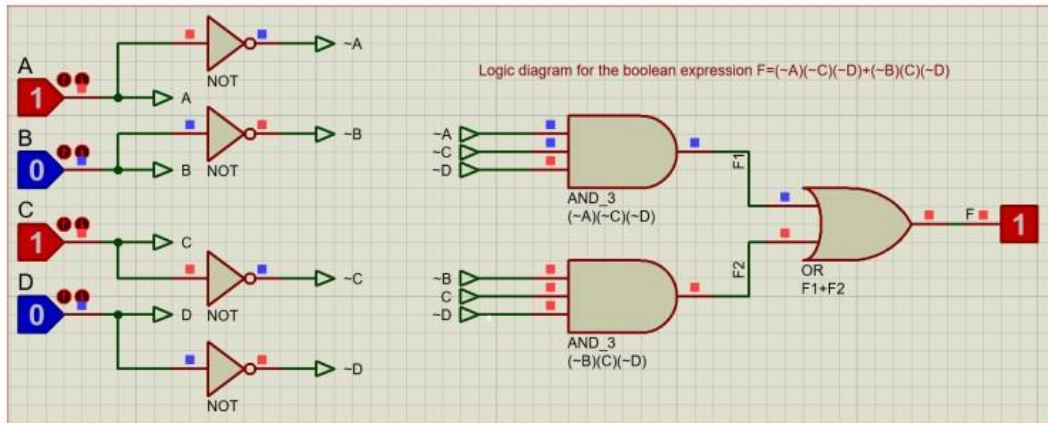

Figure(12): F2 logic diagram