



Faculty of Engineering and Technology
Electrical and Computer Engineering Department

DIGITAL INTEGRATED CIRCUITS



Assignment 2


Name: Aya Dahbour

ID: 1201738



Instructor: Khader Mohammad

1- Build N-latch schematic and layout.

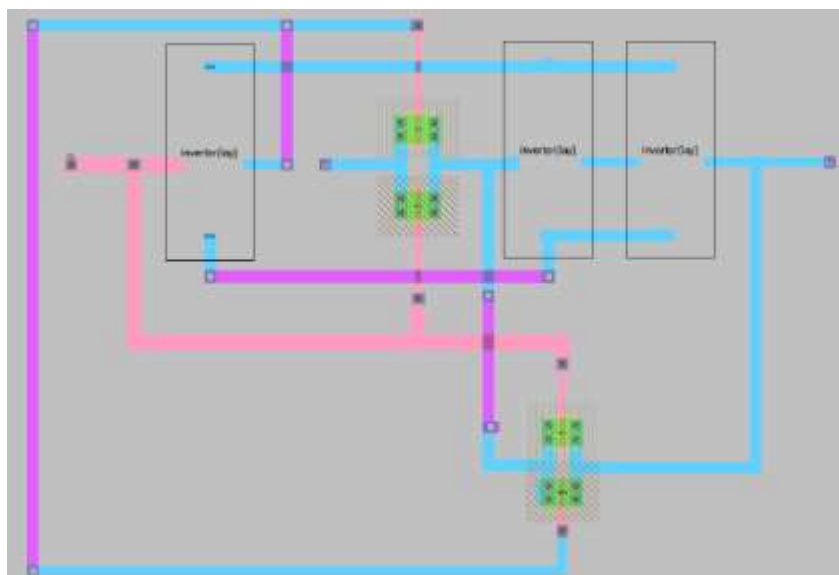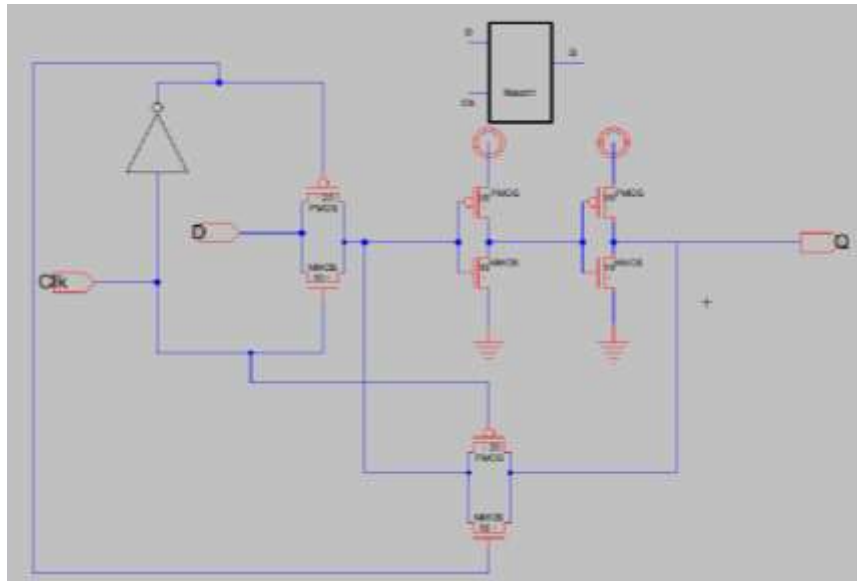

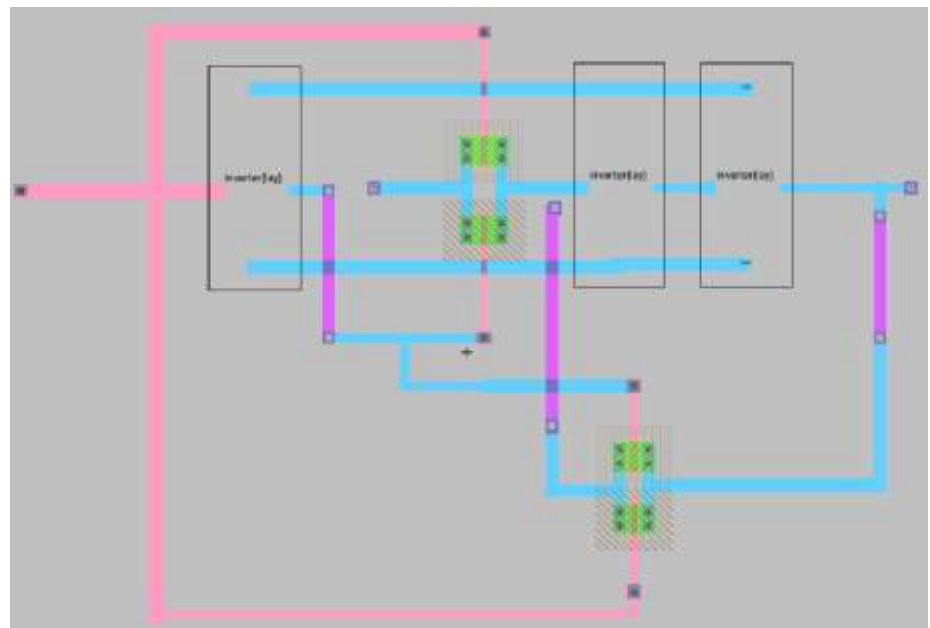

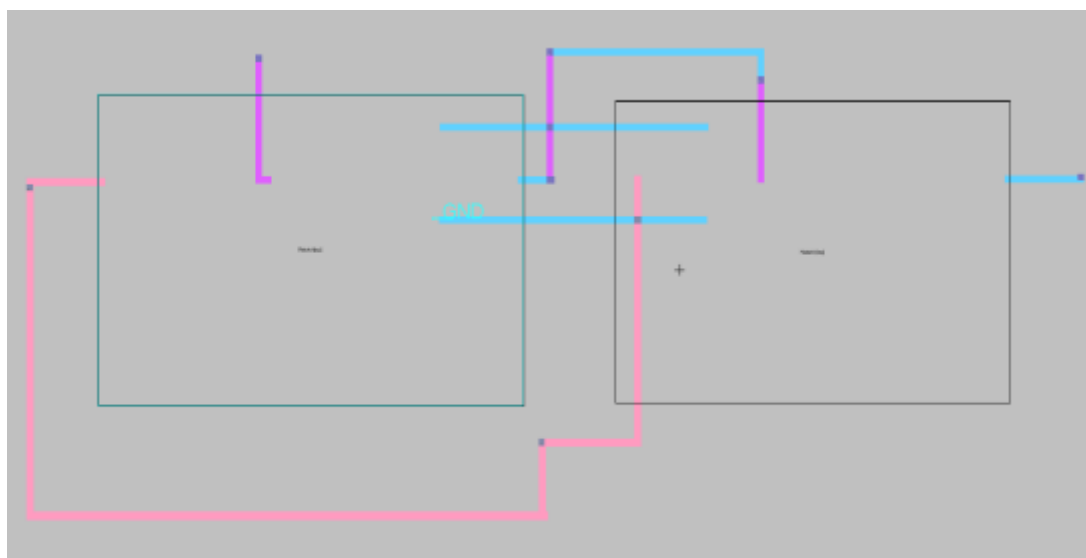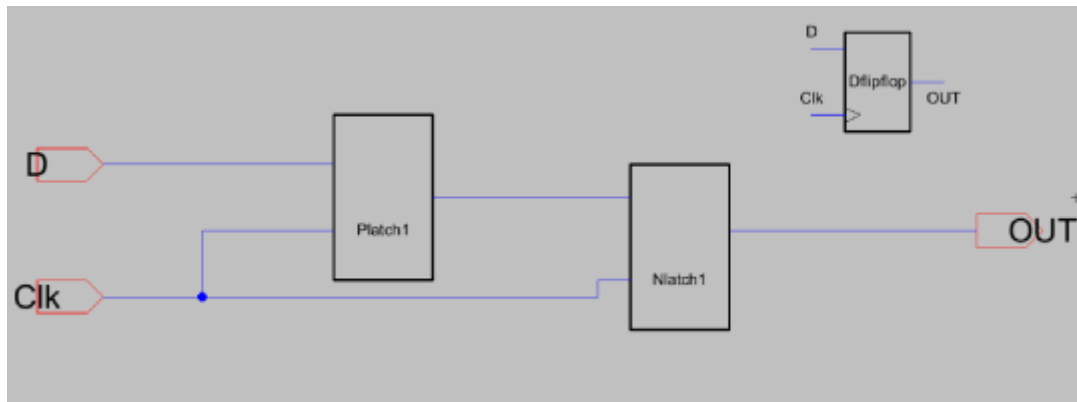3- Build a rising edge Flip-Flop schematic and layout.



4- Build a falling edge Flip-Flop schematic and layout.

