



Faculty of Engineering and Technology

Electrical and Computer Engineering Department

Digital Lab (ENCS2110)

Experiment No.6 Pre-Lab

Title: Sequential Logic Circuits Using Breadboard

Prepared by:

Name: Aya Dahbour

Number: 1201738

Instructor: Dr.Bilal Karaki

TA: Eng. Ali Hamoudeh

Section: 2

Date: 12/5/2022

Q1:

What is the appropriate display type (common anode/common cathode) that must be used with 7447 display decoder? Why?

Answer: the outputs of 7447 IC are active low. Regarding to the definitions of common anode/common cathode, the appropriate display type is common anode because the inputs of LED segment must be active low.

Q2:

We would like to limit the current in the LED segments to 10mA. Assuming that the turn-on voltage for the LED's is 1.7v, what is the proper value of the resistors to be connected between the 7447 decoder and the 7-segment display?

Current in the led segment = 10 mA

Turn-on voltage for the LED = 1.7 v

V_{cc} = 5 v

V_{cc} – turn-on voltage - V_R = 0

5 – 1.7 = V_R

According to ohm's law: V_R = IR

V_R = 3.3 v → V_R = IR → $R = \frac{V_R}{I}$

$R = \frac{3.3}{10 \times 10^{-3}} = 330 \Omega$

Q3:

Assume that the resistors provided in the lab are 220Ω . What would the current flowing into the LED's be?

$$R = 220\ \Omega$$

$$V_R = 3.3\ \text{v (calculated in Q2)}$$

$$\text{Ohm's law: } V_R = IR$$

$$3.3 = 220 * I$$

$$I = 15\ \text{mA}$$

Q4:

Design a decade counter circuit using the 7490 counter, the 7447 decoder, and a 7-segment display. Show the pin numbers on the IC's in your design

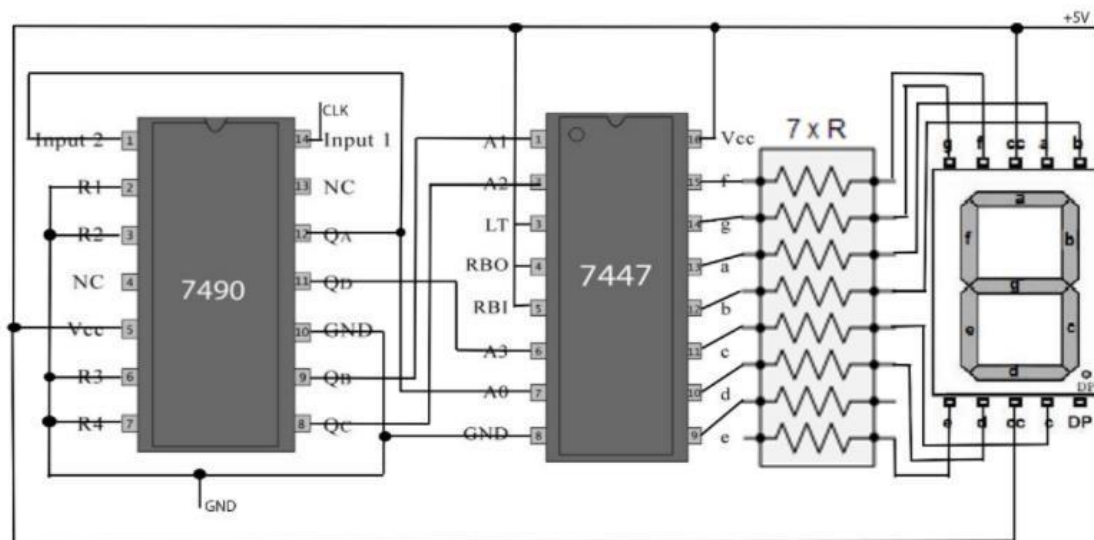


Figure 1: Decode counter circuit