



Faculty of Engineering and Technology

Electrical and Computer Engineering Department

Digital Lab (ENCS2110)

Experiment No.4 PostLab

Title: Digital Circuits Implementation using Breadboard

Prepared by:

Name:Aya Dahbour

Number:1201738

Instructor: Dr. Bilal Karaki

TA: Eng. Ali Hamoudeh

Section: 2

Date:5,May,2022

Post Lab:

A 3-to-8 decoder can be built using two 2-to-4 decoders plus some basic logic gates as shown in the following figure.


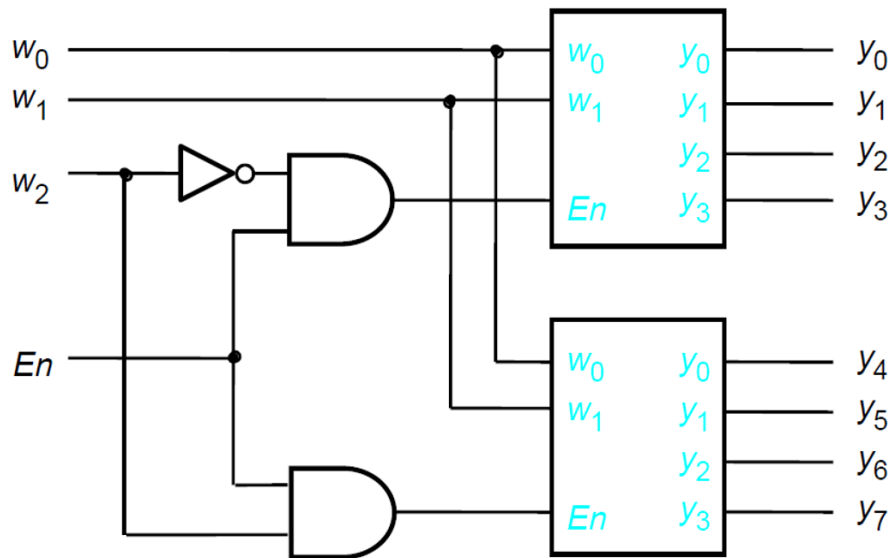


Figure 1:3X8 decoder with enable

HomeWork:

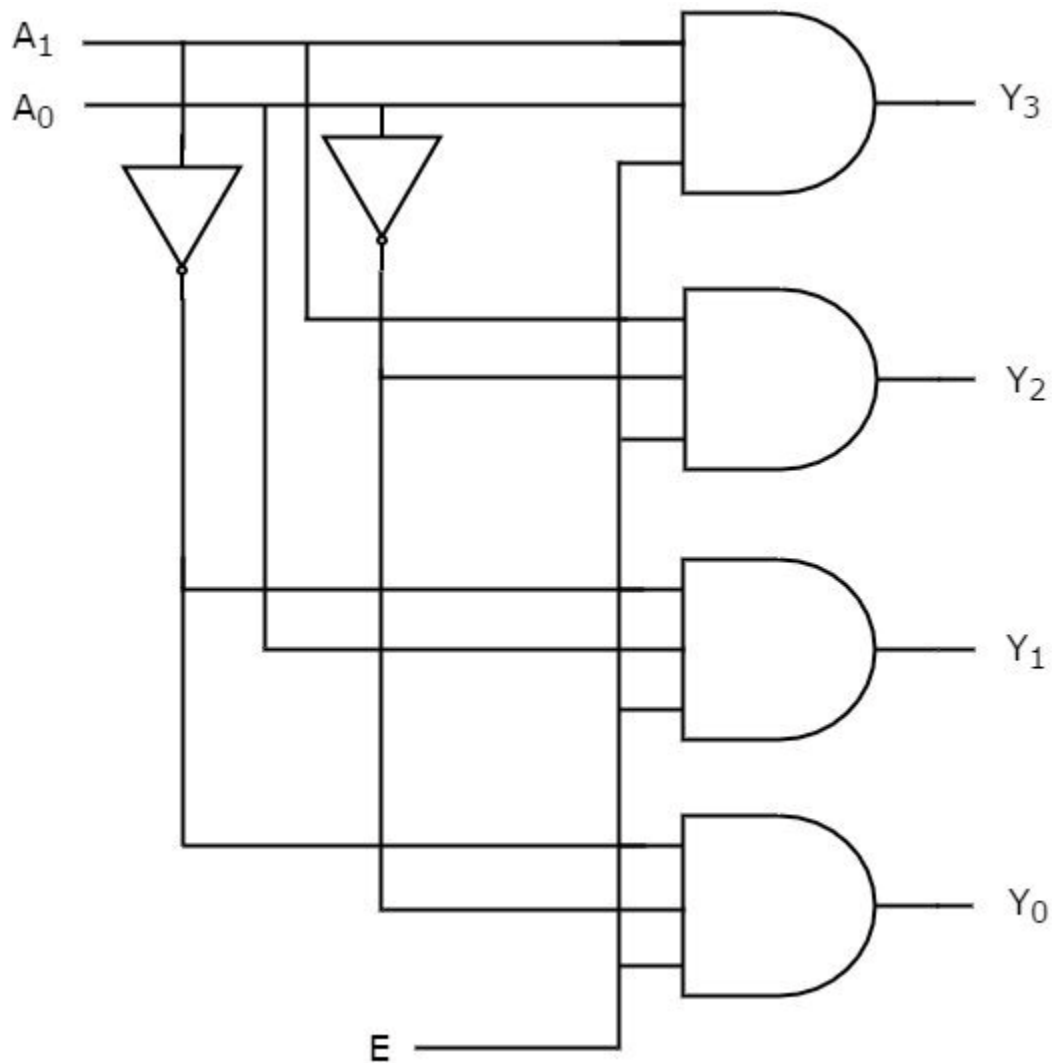2.a: How do you go about adding an Enable (E) signal to the decoder?



3.a:

Use the just constructed 4x1 multiplexer to design a three inputs network that gives 1 if the majority of its inputs are 1 and outputs a zero otherwise .

Sensor Inputs			Output
A	B	C	
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$\bar{A}BC = 1$
 $A\bar{B}C = 1$
 $AB\bar{C} = 1$
 $ABC = 1$

$$\text{Output} = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

