



**Faculty of Engineering & Technology Electrical & Computer Engineering
Department**

Circuits and Electronics Laboratory - ENEE2103

**PreLab Exp7: BJT Transistor As An Amplifier, CE, CC,
CB Connection**

Prepared By:

Aya Dahbour 1201738

Instructor: Dr. Nasser Ismail.


Assistant: Eng. Bilal Ismail

Section: 3


Date: 20/12/2022

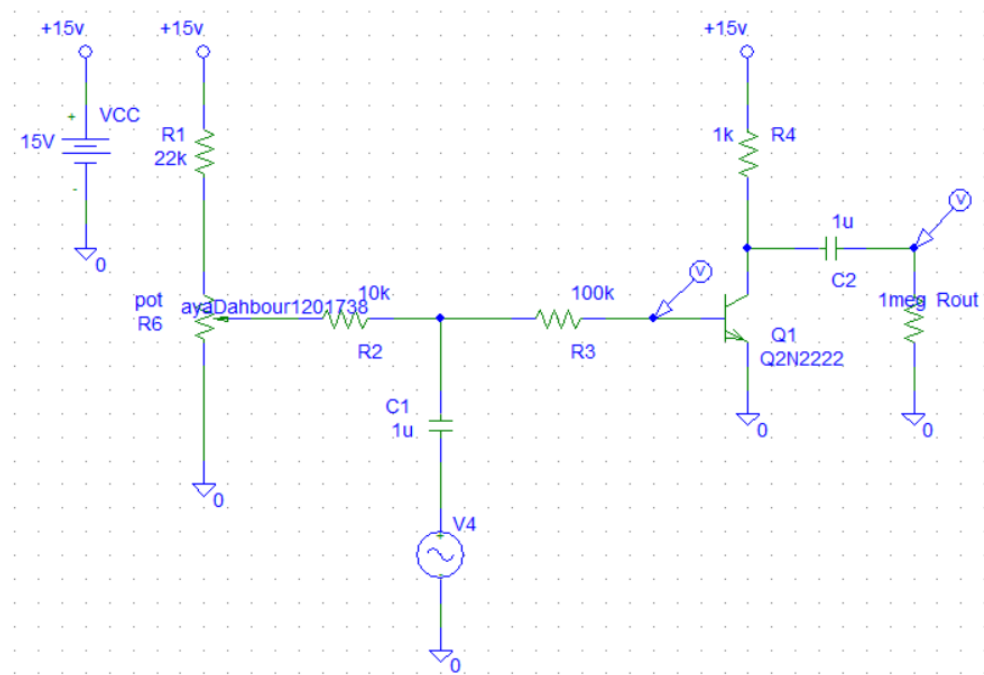Part 1 :

The circuit connected in Pspice as follows :



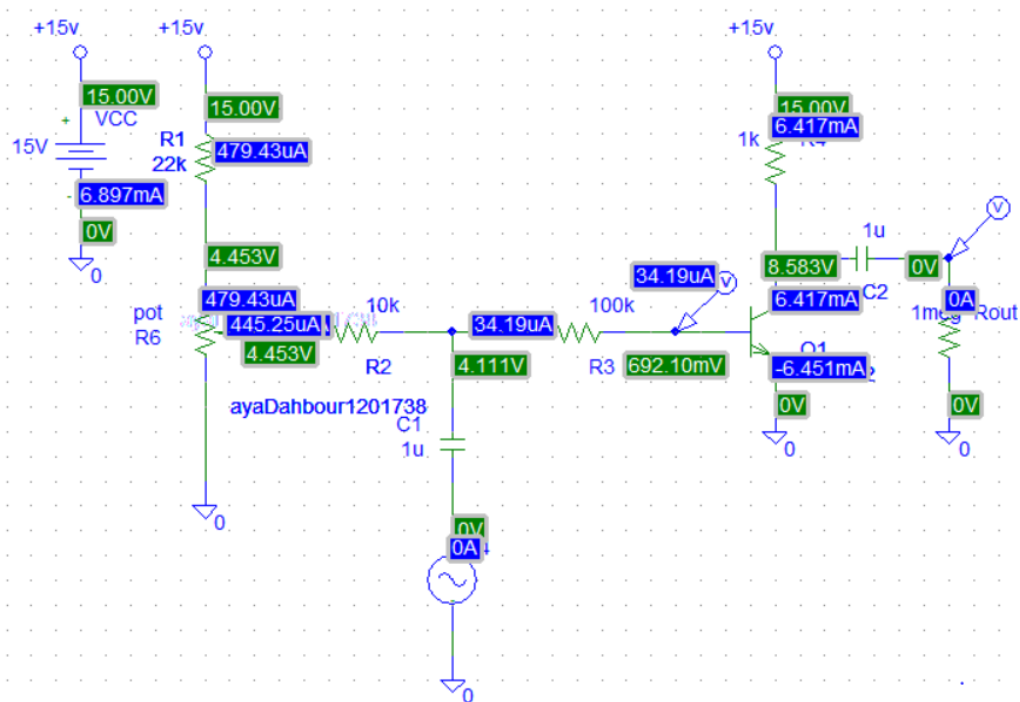Then set $V_i(t)$ amplitude to 0, set the potentiometer value to 10 k and its set value to 0. And sinusoidal source to 1 kHz and amplitude to zero.



$$V_C = 8.5383\text{v}$$


$$V_{BE} = 0.692\text{v}$$

$$V_{CE} = 8.583\text{v}$$

$$I_C = 6.417\text{mA}$$

$$I_B = 34.19\text{uA}$$

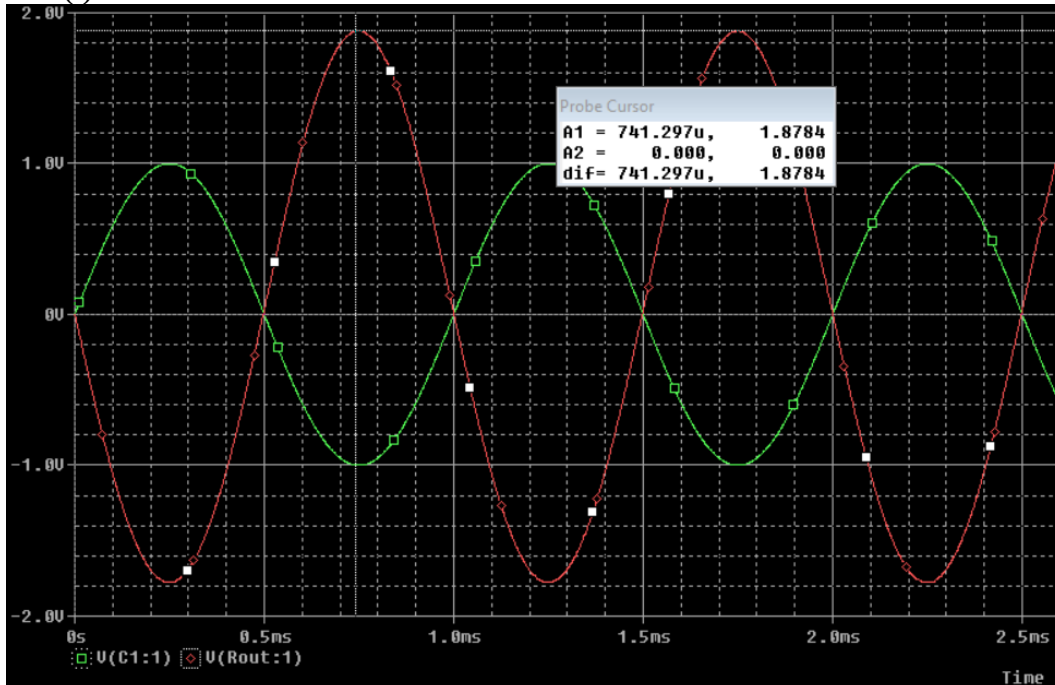
Then adjust amplitude of $V_i(t)$ to 1 V
 $V_o(t) = 1.8784\text{v}$



Change peak of $V_i(t)$ such that $V_o(t) = 4\text{V}$ peak and perform Transient analysis

to find V_i : $1.8784 = 4 / V_i$ so $V_i = 2.15\text{v}$ then adjust amplitude of $V_i(t)$ to 2.15 V



$V_o = 4.085\text{v}$

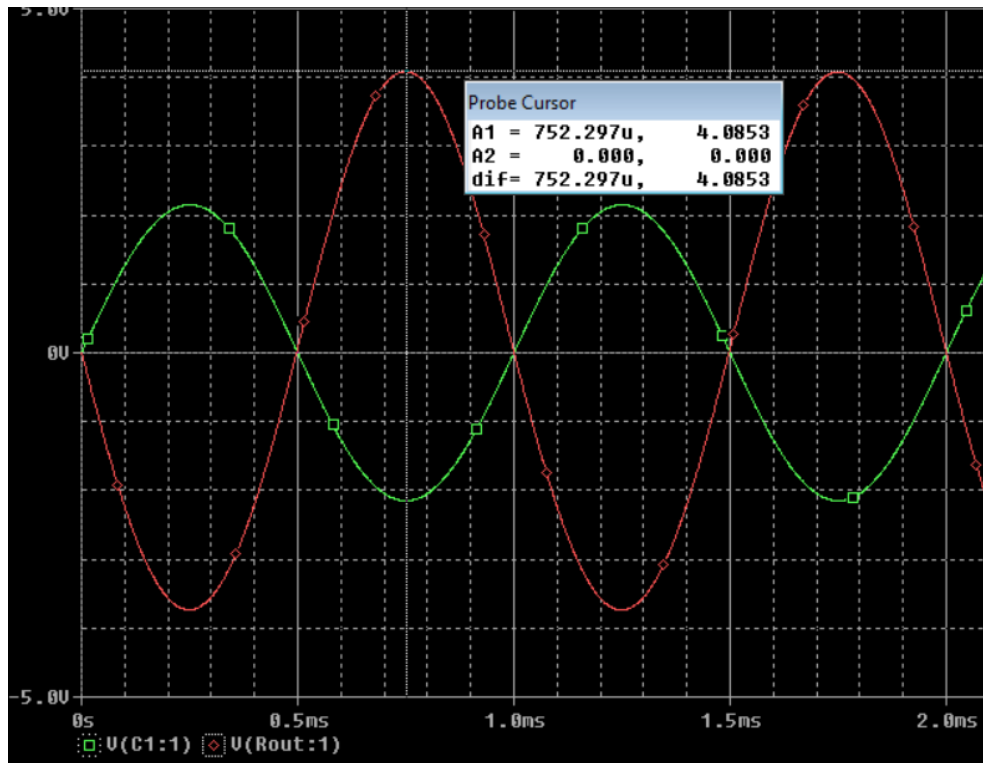

the voltage gain of the transistor $A_v = V_o(t) / V_i(t) = 4.085 / 2.15 = 1.9$

$$A_{v1} = V_o(t) / V_B(t) = 4.085 / 0.692 = 5.9$$

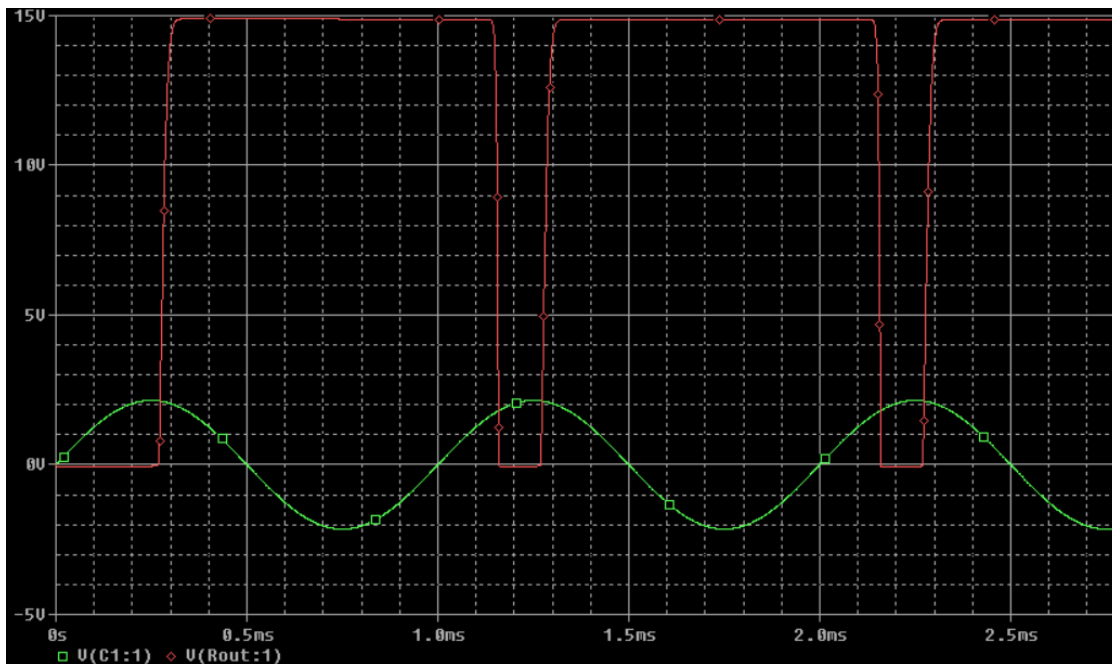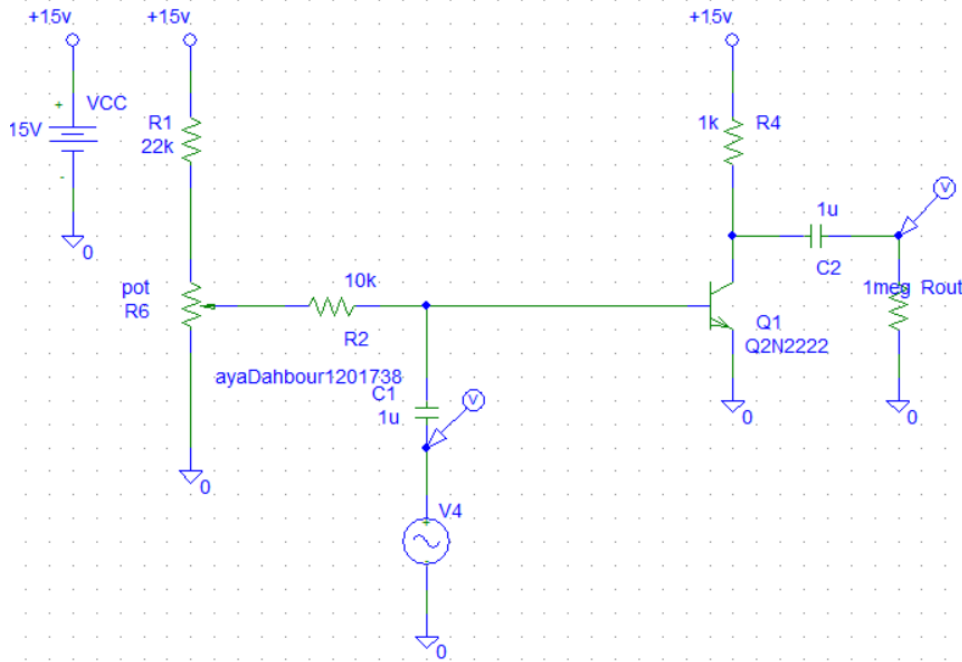** Remove the 100k resistor and see what happens to voltage gain :




$$A_v = V_o(t) / V_i(t) = 15 / 2.15 = 6.976$$

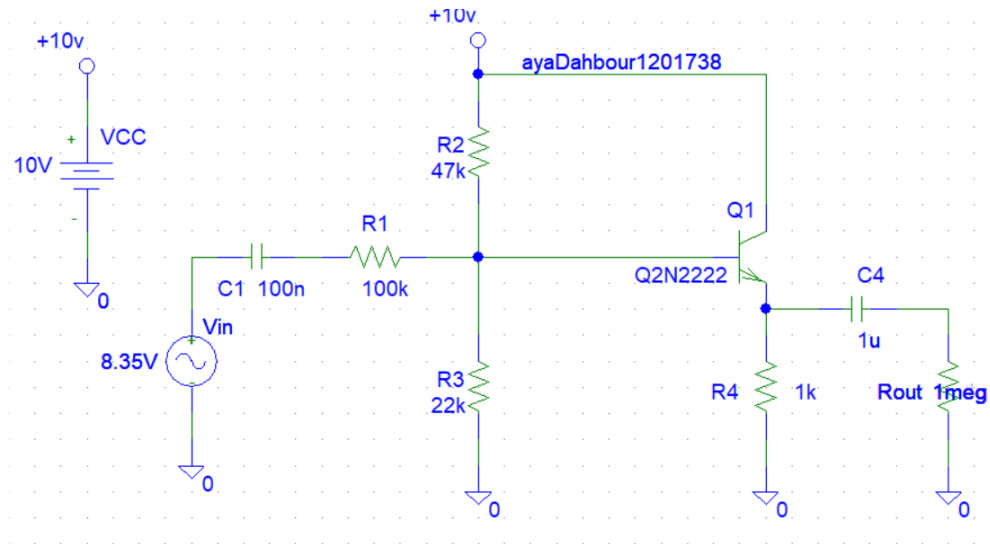
Part 2 :

COMMON COLLECTOR TRANSISTOR AMPLIFIER


The circuit connected in Pspice as follows :




Set the sine wave generator to a frequency of 1 kHz , and its output amplitude to zero

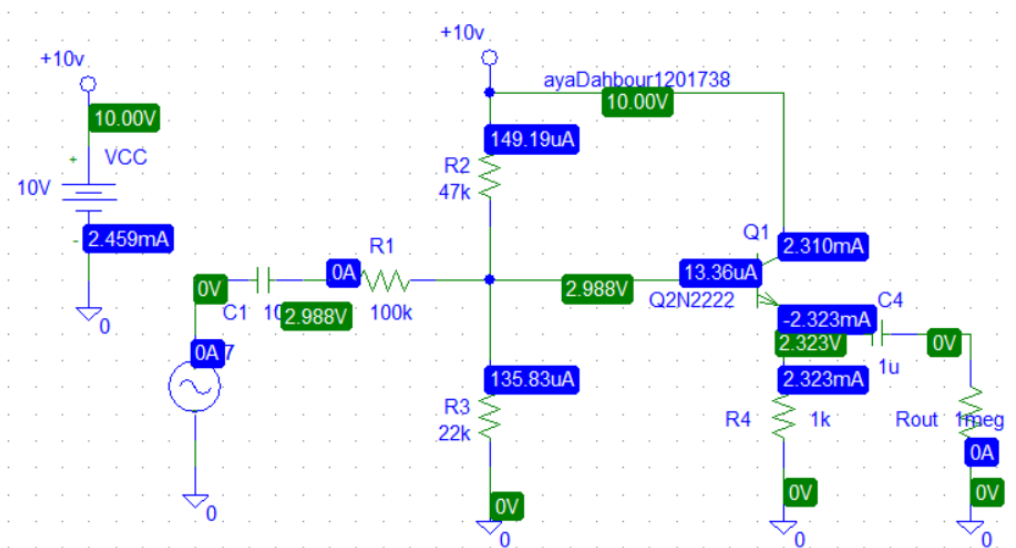
$$V_B = 2.988\text{V}$$
$$V_C = 10\text{V}$$
$$I_B = 13.36 \mu A$$
$$I_C = 2.31 \text{ mA}$$

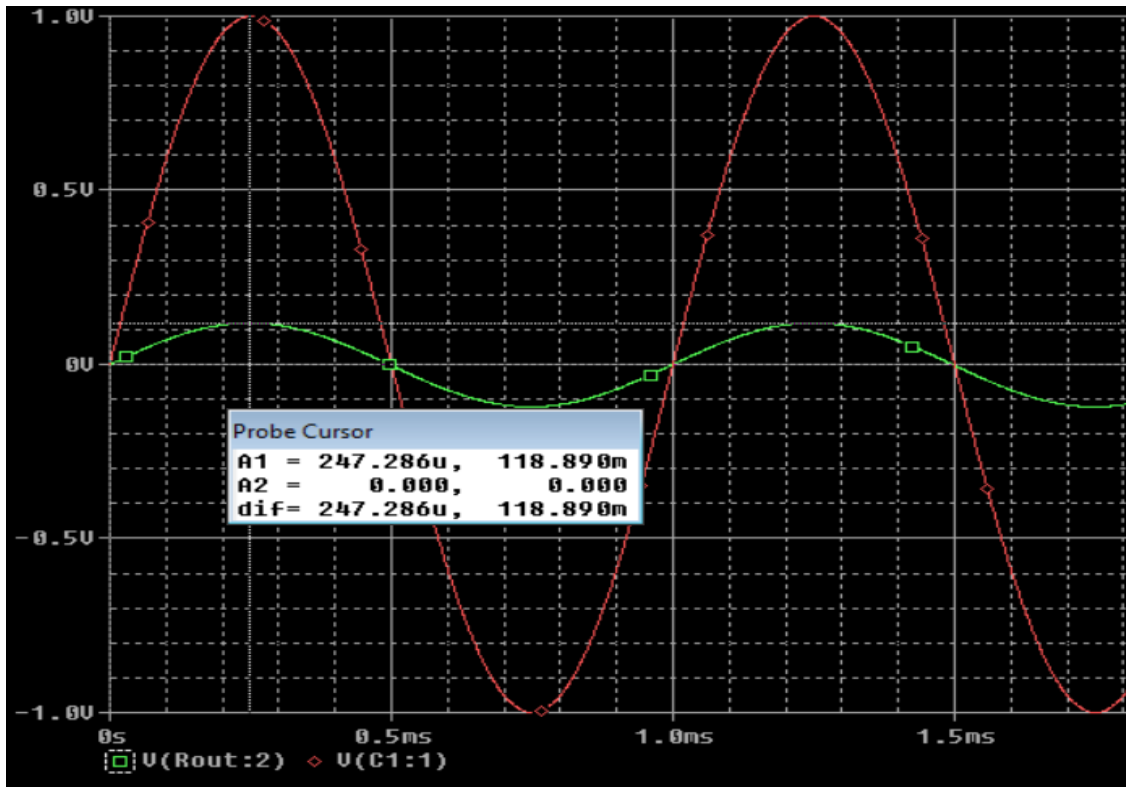Adjust the amplitude of the sine wave generator until an output amplitude from the amplifier is about 2 volts peak-to-peak.



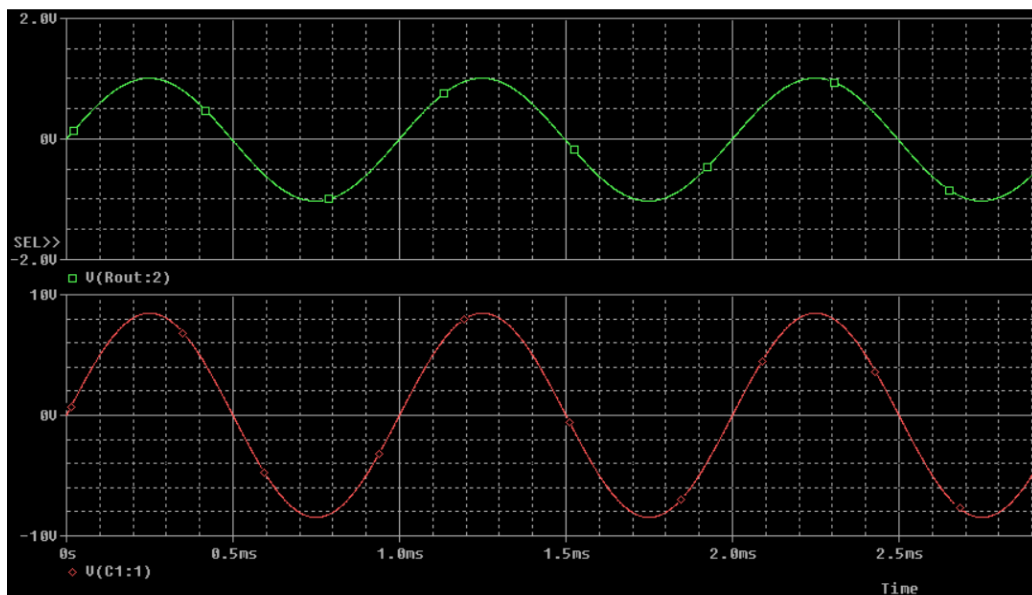
>>> 1v peak , To get 1v : $V_i = 1/0.118 = 8.47v$



the voltage gain $A_v = V_o/V_i = 1/0.118 = 8.47$

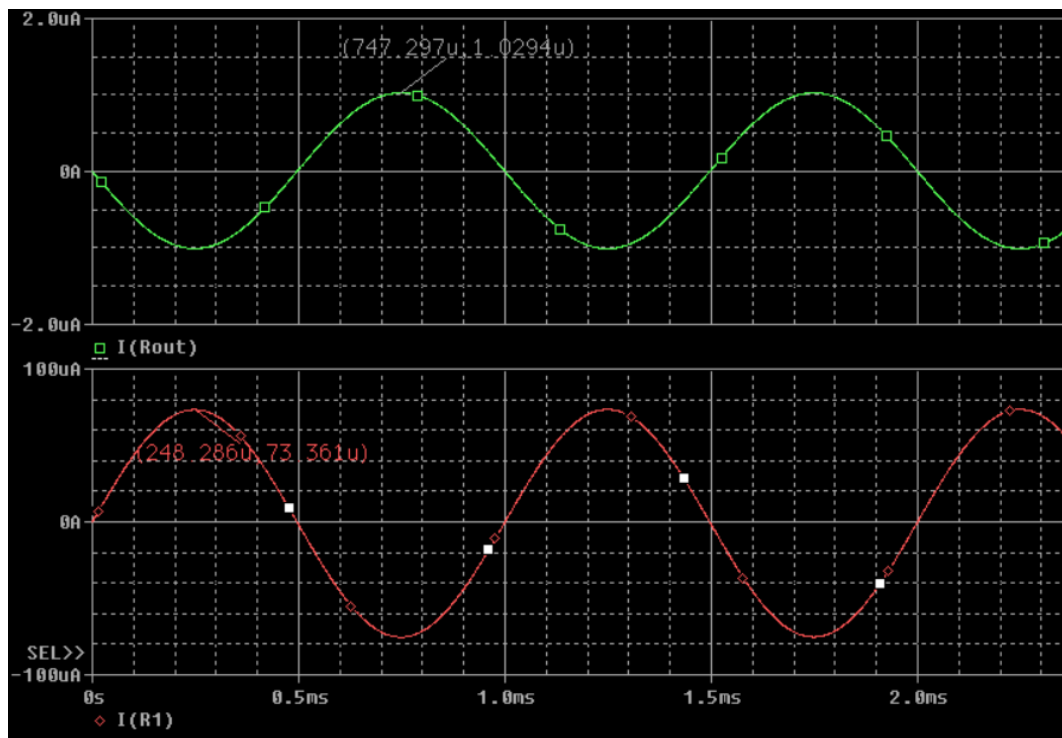
The input and output currents are displayed as shown below :




$I_{in} = 73.361\mu A$ amplitude, $I_o = 1.074\mu A$, so the current gain $A_i = I_o/I_{in} = 1.074/73.361 = 14.63$ m

$Z_i = V_{in} / I_{in} = 8.47/73.36\mu = 115458 \Omega$

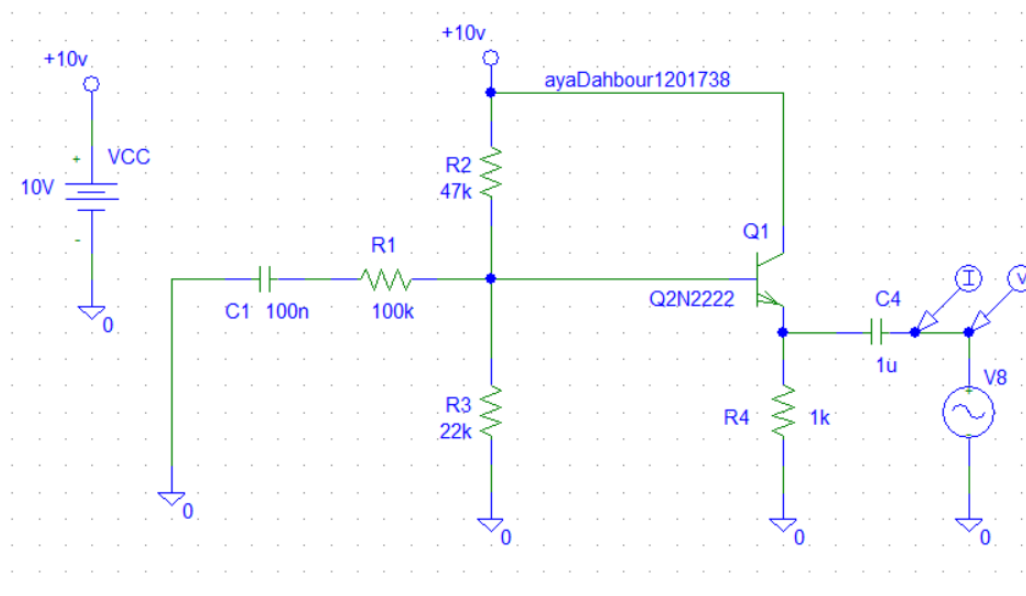Finally find the output impedance of the amplifier :



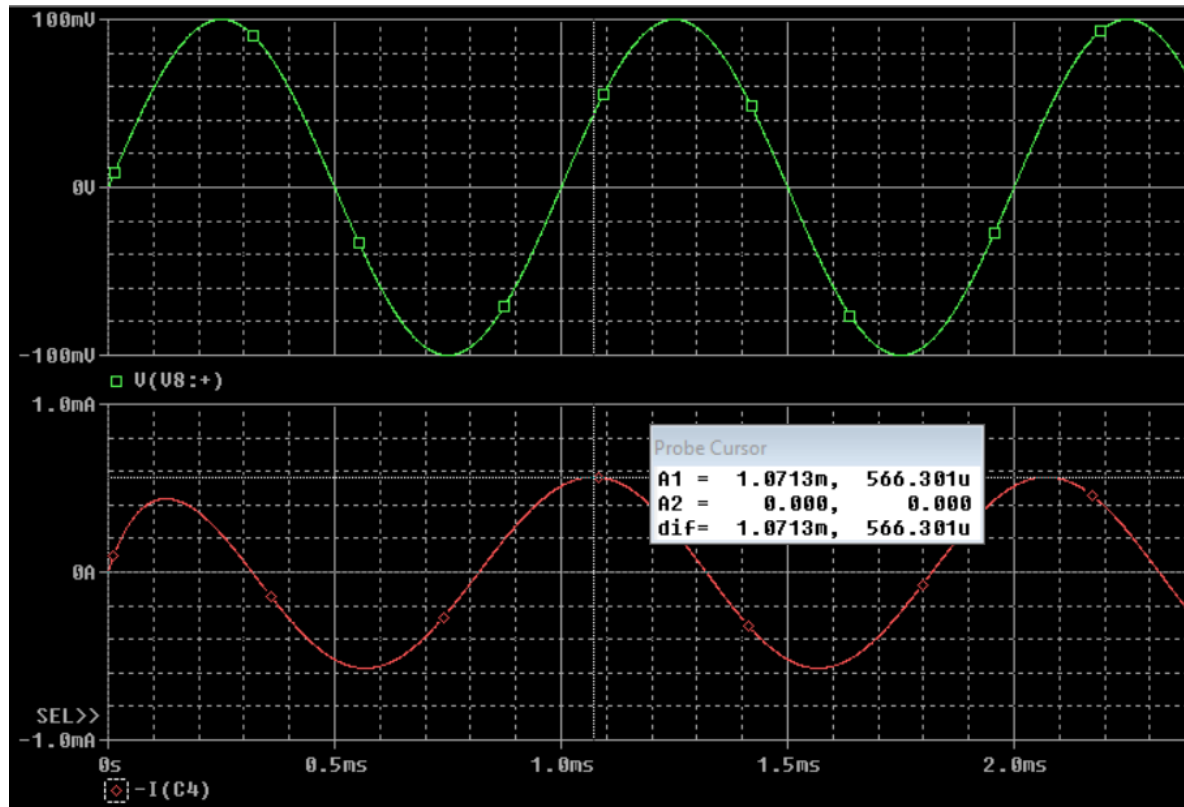The plots of the current and voltage are both displayed in the figure below as the voltage is in green and the current is in red.



$$Z_o = V_o/V_{in} = 100m/566.3u = 176.5 \, \Omega$$

Quantity	Measured values
V_{in}	8.47v
V_{out}	1v
V_{100k_RMS}	7.2929v
i_{out}	1.074uA
	Calculated values
$A_v = V_{out}/V_{in}$	0.118
$i_{in} = V_{100k_RMS} / 100k$	72.929uA
$A_i = i_{out}/i_{in}$	14.36m
$Z_{in} = V_{in}/i_{in}$	115458
$Z_{out} = V_T/i_T$	176.5